

James Solonika  
EET 256 Capstone  
Progress Report  
Week 5

## IC Tester

### Current functionality -

Two counters run through all combinations for an 8 input 7400 series logic chip.  
Microcontroller verifies whether the output is correct for an AND chip or not using logic tables stored in EEPROM

### Problems -

Took longer than expected to create and program all 5 256 value logic tables.

### Next Weeks Steps -

Have microcontroller compare the chip output to a table of different logic values (OR, NOR, NAND, etc.) to see which chip it is

### Percentage complete -

Hardware prototyping - 85%

Software - 50%

Manufacturing - 0%

### Hardware log since last week –

4/26/15

Micro controller now controlling counters instead of hand.

Added more LEDs to indicate all logic types (AND, OR, NAND, NOR, XOR)

### Software log since last week –

3.0: 4/27/15

Created an EEPROM programmer to store 4 full data tables (1024 bytes available, 4 256 byte truth tables). One chip table will have to be stored in local memory each time, but this should speed up setup time on the device. (5 logic chips - AND, OR, NAND, NOR, XOR, only 4 can fit in EEPROM)

Created all 5 truth tables. XOR is programmed into run code.

3.1 4/30/15

Added interrupt code to run program when a button is pressed

